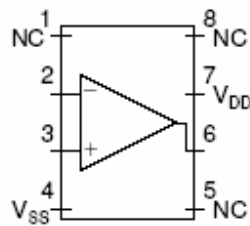



MASSACHUSETTS INSTITUTE OF TECHNOLOGY
6.071 Introduction to Electronics, Signals and Measurement
Spring 2006

Laboratory 23: Schmitt Trigger Oscillator

Using the LF356 op-amp the pinout of which is shown below,



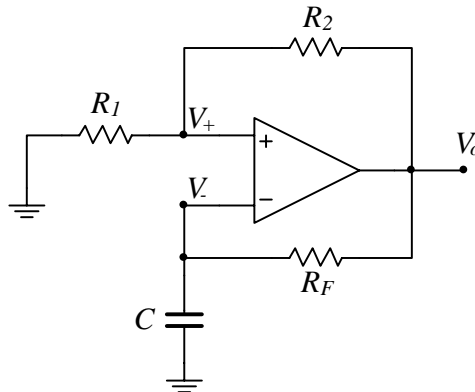1. Design, build and test a square wave generator oscillating at a frequency of 1kHz and a duty cycle of ~50%



With what voltage(s) would you power the op-amp?

Calculate the list the values you would use for the following components:

R1:

R2:

RF:

C:

Use the scope to observe V_o and V_- and draw the signals below.



2. What is the highest frequency square wave that you can generate with this circuit? (Try changing C in decades and observe the result.) What would the signal V_o look like at high frequencies? Can you explain the reason for this behavior?
3. Modify the circuit so that the square wave can have variable duty cycle. (Hint: use your $20\text{k}\Omega$ variable resistor to change the voltage level that powers your op-amp) What is the basic idea here?

Show your circuit schematic below.

Vary the potentiometer and observe the signals V_o and V_- .