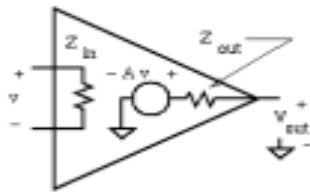


Operational Amplifiers



Parameter	Ideal	'741	'357
Int Gain	A	Infinity	200,000/f(Hz)
Output Impedance Z _{out}	0	~75 Ohms	
Input Impedance Z _{in}	Infinity	~300 kOhms	~10 ¹² Ohms



Uses of Op Amps



Analog uses employ negative feedback to drive + input to (nearly) the same potential as the - input

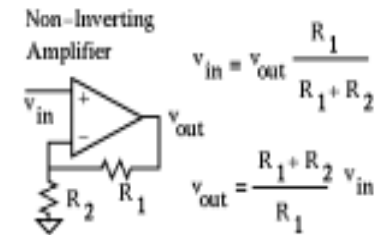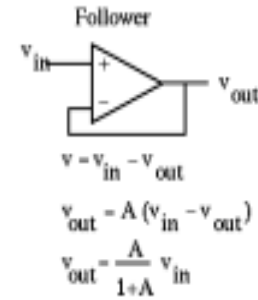Follower and Non-Inverting Amplifier Circuits:





More Analog Circuits

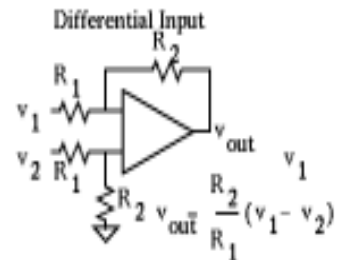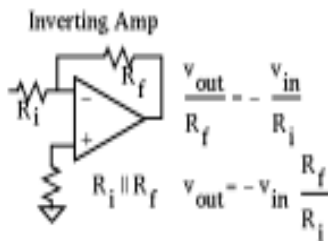Inverting Amplifier and Differential Input Amplifier




Positive Feedback

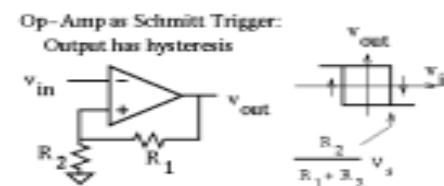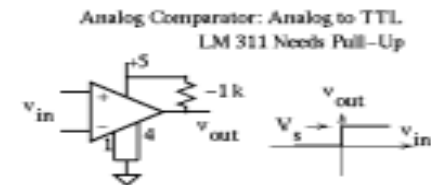Analog Comparator
 Is $V_+ > V_-$?
 Output is a DIGITAL signal
 Schmitt Trigger squares up signals



Bias Currents

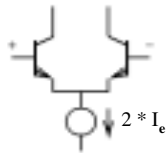Many Op-Amps have bipolar inputs
 Emitter coupled transistor pair
 High differential gain
 But sum of input currents = I_e/β



Many Op-Amps have FET inputs
 Bias currents are very small


Pinouts: 8-pin "mini-dip"

Common packaging

- Pin 3 Positive Input
- Pin 2 Negative Input
- Pin 6 Output
- Pin 7 Positive Supply
- Pin 4 Negative Supply


You may need these pinouts:

8-Pin "Mini-Dip"

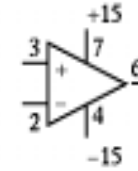


Slew Rate

Is related to frequency response

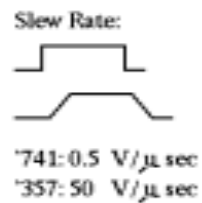


Summing Junction

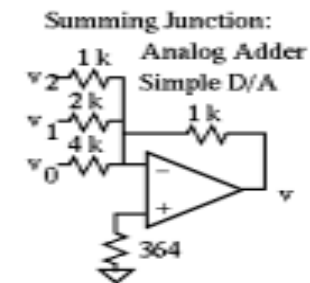If V_+ is at zero potential, so is V_- (assuming negative feedback)
 Output voltage is proportional to sum of currents
 Currents are inversely proportional to resistances, IF voltages are the same




Useful Circuit

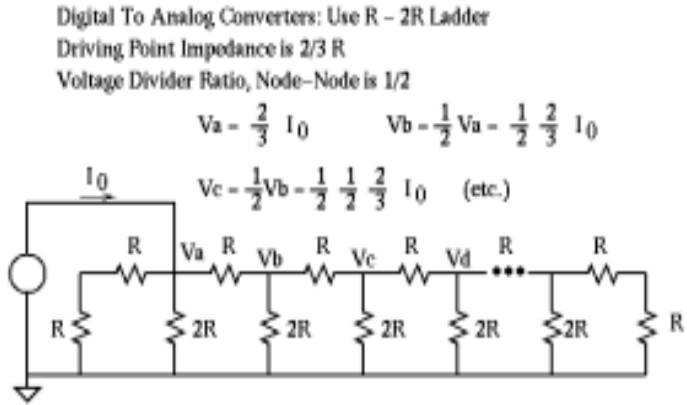

9


How to build a D/A

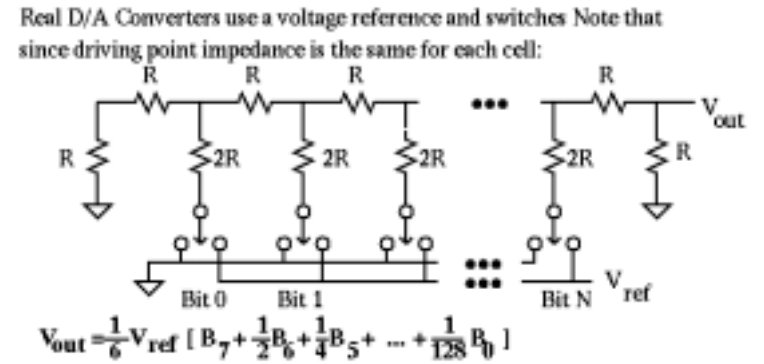

10

AD 558

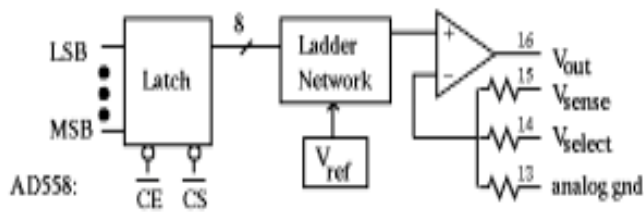
8-Bit D/A Converter
 You will use in Lab 3



11

Control of AD 558

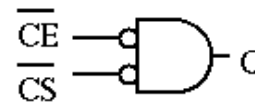
Is relatively simple
 Remember -- This is a LATCH
 Data goes through to analog when G is HIGH
 Output can be very noisy when bits are settling
 (particularly if the source is something like memory)



12

Output of AD 558

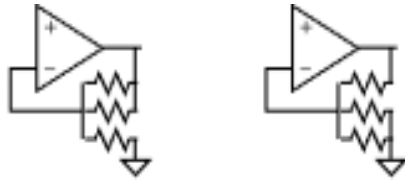Much like a Non-Inverting Operational Amplifier
 Left circuit goes 0 to 2.5 volts
 Right circuit goes 0 to 10 volts
 Needs 12 volt power supply!



Analog to Digital Conversion

Harder than Digital to Analog

Several Different Methods are Used: (here are three)

Dual Slope Integration

Uses time which can be measured accurately
 Typically very accurate but slow
 Not widely used any more

Multiple Conversions (FLASH)


Very fast
 Used for converting TV signals
 Difficult to make in high precision
 AD 775

Successive Approximation

Medium speed
 Can be economical
 AD 670


Dual Slope

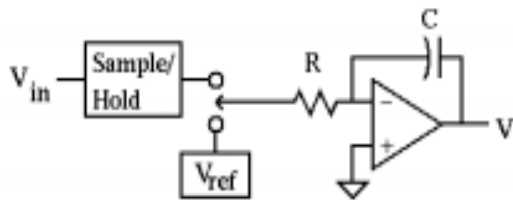Dual Slope Integrating A/D
 Accurate but slow
 Requires accurate integrator
 And accurate counter and clock




Operation of Dual Slope

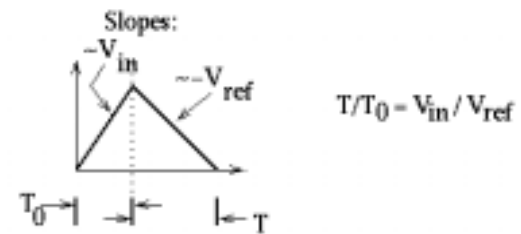First, Counts
 for known time
 with input voltage at input to the integrator
 Then counts
 with reference voltage at input
 and measures time




Flash Converter

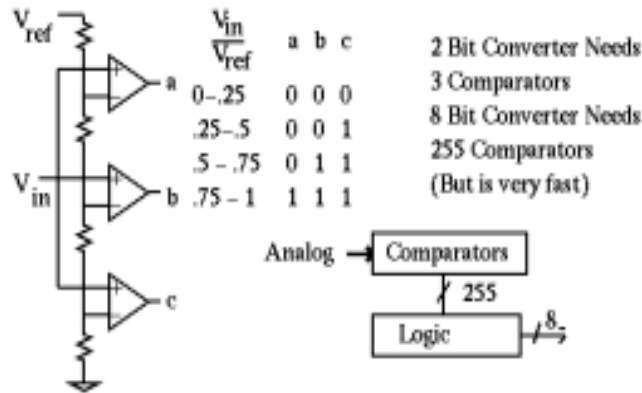

17

AD 775 Functional Block Diagram

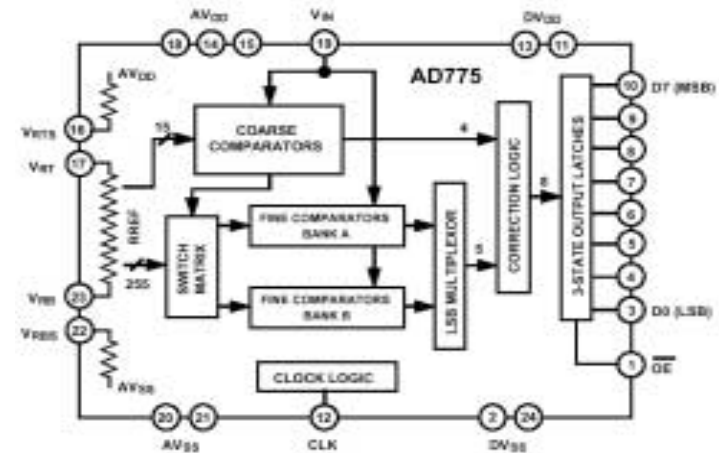


18

AD 775 Timing: Samples on falling edge, data available on rising edge, 2 1/2 clock cycles later.

TIMING SPECIFICATIONS

	Symbol	Min	Typ	Max	Units
Maximum Conversion Rate		20	35		MHz
Clock Period	t_{clk}	20			ns
Clock High	t_{clkH}	25			ns
Clock Low	t_{clkL}	25			ns
Output Delay	t_{out}		18	30	ns
Pipeline Delay (Latency)				2.5	Clock Cycles
Sampling Delay	t_{sp}		4		ns
Aperture Jitter			30		ps

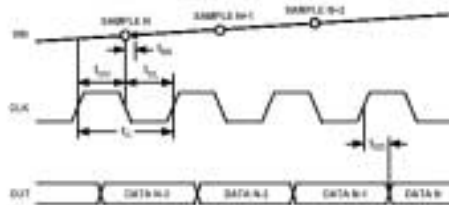Specifications subject to change without notice.




19

Voltage Reference

Similar to other flash converters
Needs a stable reference voltage
Can handle different Ranges of voltage defined by top and bottom of ladder

Caution is required: the ladder is fragile!

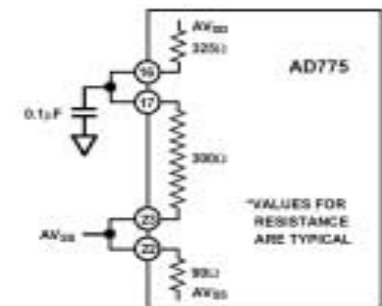
Voltage range < 2.8 volts
Linearity suffers if < 1.8 volts
AV means "Analog Voltage" (supply)
If you use this converter, get AV_{DD} set BEFORE connecting to the A/D converter



20


Successive Approximation A/D

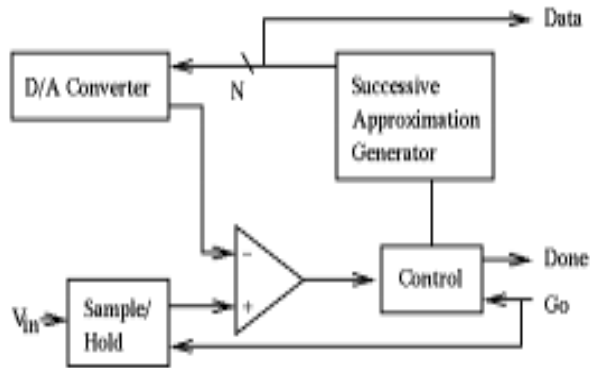Widely used in low and medium frequency applications (such as audio)




Operation of Successive Approximation A/D

Set one bit at a time
 D/A generates analog voltage
 Compare with input
 If overshoot, turn that bit on
 Finishes in fixed time

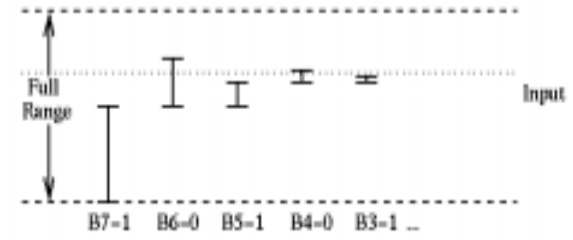


AD 670

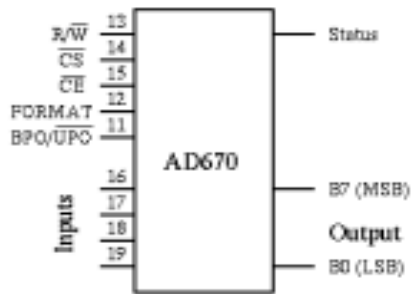Conversion time 10 microseconds
 Internal voltage reference
 Multiple input ranges
 Two output formats



Control Logic for AD 670

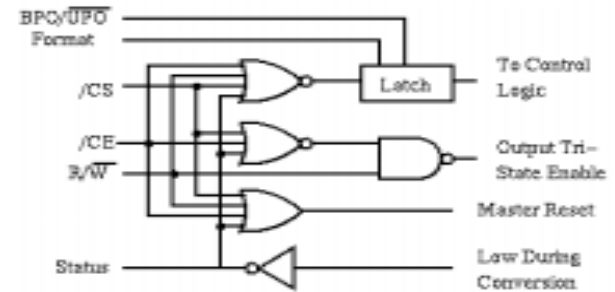


Mode Control:

BPO/UPO	Format	Input Range	Output
0	0	Unipolar	Binary (unsigned)
1	0	Bipolar	Binary (unsigned but offset)
0	1	Unipolar	2's Complement
1	1	Bipolar	2's Complement

AD 670 Can Handle Multiple Input Ranges

High Input Voltage Range
 0 to 2.55 V or
 -1.28 to +1.28 V
 Strap Pins 17 and 18 to GND
 Input is Pins 16 (+) and 19 (-)

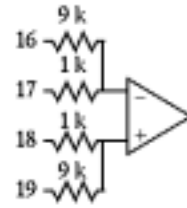
Low Input Voltage Range
 0 to 255 mV or
 -128 to +128 mV
 Strap Pins 16 to 17 (+)
 and 18 to 19 (-)



25

Timing: Single Conversion Cycle

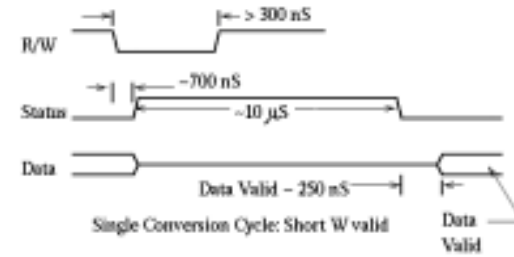Assumes /CS and /CE are LOW
 Need to control these if connected to a bus!
 Conversion initiated by R/W LOW pulse




26

Timing: Multiple Conversion Cycles


Here is what happens if you hold R/W low

Must wait for last conversion to finish

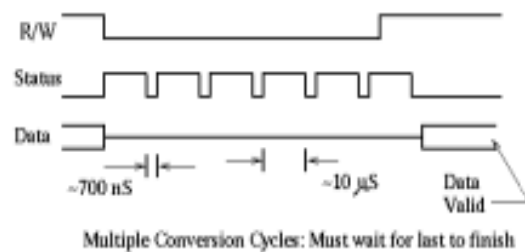

27

A/D, D/A and Aliasing Demo

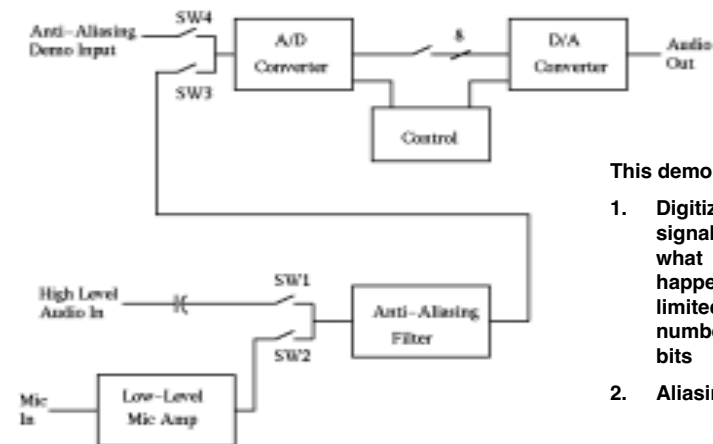


This demo shows:

1. Digitized signals (and what happens with limited number of bits)
2. Aliasing


28

Control and Digital Section

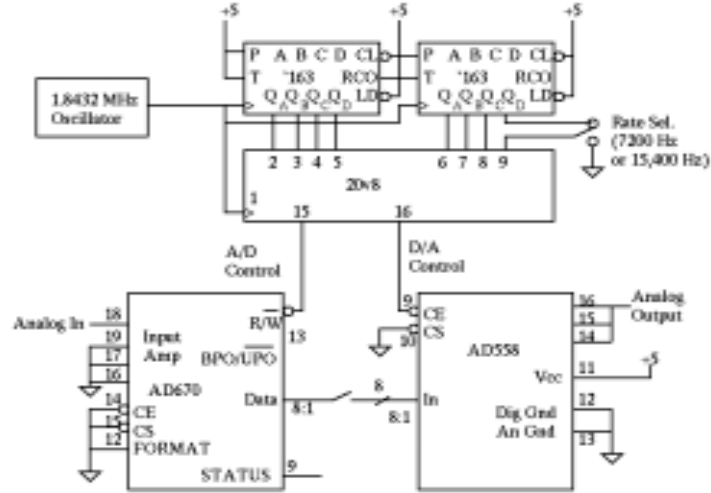

29

Analog: Gain and Anti-Aliasing

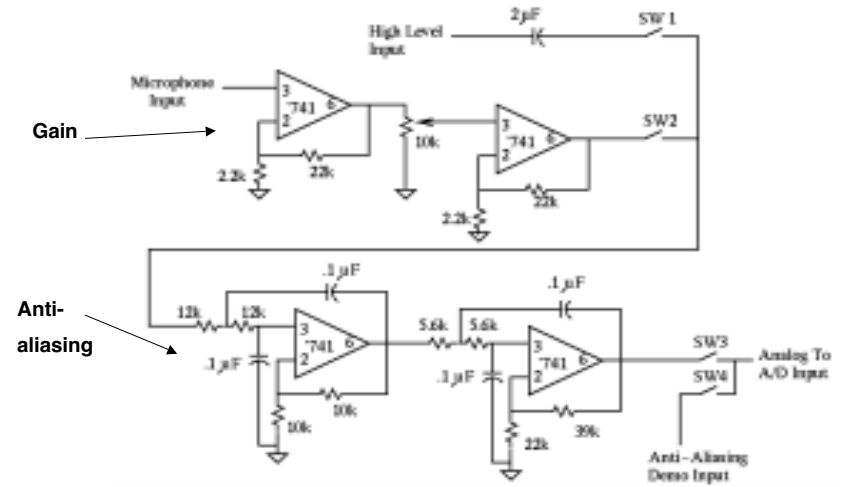

30